

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV(NEW) EXAMINATION – WINTER 2022****Subject Code:3140913****Date:15-12-2022****Subject Name:Electrical Machine- I****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed

	MARKS
Q.1 (a) Explain principle of energy conservation.	03
(b) List out parts of D.C machine and briefly discuss any two.	04
(c) A shunt generator deliver 195A at 250V, armature and shunt field resistances are 0.02Ω and 50Ω respectively. The iron and friction losses are 950W. Calculate (1) Emf generated ,(2)Total copper loss,(3)Output of prime-mover,(4)Mechanical efficiency , electrical efficiency and total efficiency.	07
Q.2 (a) Define following terms: (1) Mechanical and Electrical angle (2) Pole pitch (3) pitch factor	03
(b) Explain polarity test of transformer.	04
(c) A 600 KVA single phase transformer has an efficiency of 92 % both at full load and half load at unity power factor. Determine its Efficiency at 60 % of full load at 0.8 power Factor lag.	07
OR	
(c) Discuss series field test on D.C machine.	07
Q.3 (a) Distinguish between singly excited and doubly excited magnetic systems.	03
(b) Define the following: (a) magnetic flux (b) mmf (c)magnetic permeability(e)leakage flux.	04
(c) Explain Equivalent circuit of transformer with circuit diagram.	07
OR	
Q.3 (a) Explain comparison between simplex lap and wave winding.	03
(b) Explain Equalizer connection.	04
(c) Define voltage regulation of a transformer. Describe the method to find out voltage regulation of a transformer using open circuit and short circuit tests.	07
Q.4 (a) Explain O.C . test on 1- Φ transformer	03
(b) Explain 3-point starter for d.c. motor.	04
(c) Explain process of commutation. Enlist different methods to improve commutation and explain any one method.	07
OR	
Q.4 (a) List the applications of d.c. motors.	03
(b) Derive condition for maximum efficiency for I - Φ transformer.	04
(c) Draw the vector diagrams and winding connections for the Following transformer connections. (a) Dz6 (b) Yz11 (c) Yd11	07

- Q.5** (a) Explain the load characteristics of d.c. shunt generator. **03**
(b) Explain Sumpner's test for testing of a transformer. **04**
(c) Explain the methods of speed control on d.c. shunt motor. **07**

OR

- Q.5** (a) Explain the conditions for parallel operation of three phase transformer. **03**
(b) What are the advantages and disadvantages of Swinburne test? **04**
(c) Derive an expression for saving of copper when auto transformer is used compared to Two winding transformer. **07**
