

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV (NEW) EXAMINATION – SUMMER 2021****Subject Code:3140915****Date:05/10/2021****Subject Name:Power Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Sketch switching characteristics of IGBT.	03
	(b) Compare IGBT and MOSFET on the basis of a) circuit symbol b) Charge carriers c) switching frequency d) Tolerance to electrostatic discharge	04
	(c) Explain working of Buck-Boost converter using circuit diagram for various modes of operation.	07
Q.2	(a) Define THD. Enlist two effects of harmonics.	03
	(b) Summarize limitations of 1- ϕ half bridge inverter.	04
	(c) Explain working of Flyback converter with circuit diagram and waveforms.	07
OR		
	(c) Explain working of Forward converter with circuit diagram and waveforms.	07
Q.3	(a) Compare unipolar sinusoidal modulation and bipolar sinusoidal modulation.	03
	(b) Explain inverter mode operation of 1- ϕ bridge rectifier.	04
	(c) Explain working of 3- ϕ inverter for 120° conduction mode using the gate voltage and phase voltage waveform.	07
OR		
Q.3	(a) Discuss SPWM technique in brief.	03
	(b) Sketch circuit diagram and waveforms of V_s , I_g , V_o , I_o and V_t for 1- ϕ full bridge controlled rectifier with R-L load with free wheeling diode.	04
	(c) Explain space vector modulation for 3- ϕ inverter.	07
Q.4	(a) Enlist methods of power factor improvement for AC-DC converters.	03
	(b) Explain principle of on-off control for AC voltage controller.	04
	(c) Explain working of 1- ϕ dual converter.	07
OR		
Q.4	(a) Explain relationship between delay angle and load angle.	03
	(b) Explain method to provide over voltage protection to power electronic switch.	04
	(c) Derive equation of output voltage for 1- ϕ AC voltage controller with RL load.	07
Q.5	(a) Derive equation of average and RMS voltage for 1- ϕ full bridge controlled rectifier with R load.	03
	(b) Explain working principle of cycloconverter.	04
	(c) Derive equation of output voltage for 1- ϕ AC voltage controller with RL load.	07

OR

- Q.5** (a) Enlist methods of SCR firing and draw circuit for any one of them. **03**
(b) Explain working principle of matrix converter. **04**
(c) Obtain characteristics of TRIAC. Explain working of TRIAC in 1- ϕ AC voltage controller. **07**
