

Enrolment No./Seat No_____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-I & II (NEW) EXAMINATION – SUMMER 2024

Subject Code:3110016

Date:06-07-2024

Subject Name:Basic Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Explain series positive clipper with diagram. 03
(b) Draw and explain V-I characteristic of P-N junction diode. 04
(c) Draw and Explain bridge rectifier. Explain advantage and disadvantage of bridge rectifier over full wave rectifier. 07
- Q.2** (a) Drive the relation between current gain α and β for CE configuration. 03
(b) Draw the symbol of NPN & PNP transistor. Also state the advantage of transistor. 04
(c) Draw and explain input and output characteristic of transistor in CE configuration. 07
- OR**
- (c) Compare CE, CB, and CC configuration with respect to different transistor characteristics. 07
- Q.3** (a) Explain V-I characteristics of tunnel diode. 03
(b) Explain Schottky diode in details. 04
(c) Comparison between P-N junction Diode and Zener Diode. 07
- OR**
- Q.3** (a) Advantage, disadvantage and application of LED. 03
(b) Compare PIN diode and Photo Diode. 04
(c) State the applications of Rectifier, and Comparison of Halfwave, Full-wave center- tap and Full-wave Bridge rectifier. 07
- Q.4** (a) List out the salient feature of emitter follower. 03
(b) Classification of Logic families in details. 04
(c) Explain application of Transistor as a switch. 07
- OR**
- Q.4** (a) Explain Negative Clamping circuit with diagram. 03
(b) Explain why NAND and NOR gate are called universal gate. 04
(c) Discuss MOSFET in details. 07
- Q.5** (a) Define the use of Coupling capacitor. 03
(b) Give Comparison of BJT and FET. 04
(c) Draw symbol and explain all logic gates in details. 07
- OR**
- Q.5** (a) Explain the properties and application of common base amplifier. 03
(b) State advantage, disadvantage and application of FET. 04
(c) Give comparison between different types of digital logic families. 07
