

GUJARAT TECHNOLOGICAL UNIVERSITY
BACHELOR OF ENGINEERING – SEMESTER 6 – EXAMINATION – SUMMER 2026

Subject Code: 3160919

Date: 01/06/2026

Subject Name: Electric Drives

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**
- 4. Simple and non-programmable scientific calculators are allowed.**

- Q.1**
- (a) Define the shunt, series and separately excited DC motor with connection diagram. **03**
 - (b) List the stator and rotor parameters of three phase induction motor and label them in approximate equivalent circuit diagram. **04**
 - (c) Discuss the advantages and disadvantages of drive control over conventional motor control. **07**
- Q.2**
- (a) Derive the equation of torque developed by separately excited dc motor. **03**
 - (b) Analyze the effect of rotor resistance variation on speed torque curve of induction motor. **04**
 - (c) Evaluate the torque speed curve of induction motor with diagram in context of applied voltage and applied frequency variation. **07**
- OR
- Q.2**
- (c) Compare the constant torque and constant power region of DC motor operation on T- ω and P- ω characteristic plane. **07**
- Q.3**
- (a) State the functions of current controller in DC motor control. **03**
 - (b) Determine the dynamic behavior of the DC drive from the torque balance equation. **04**
 - (c) Analyze the slip power recovery system with diagram in context of efficiency improvement of three phase induction motor. **07**
- OR
- Q.3**
- (a) State the principle and applications of scalar control of induction motor. **03**
 - (b) Show that the SVPWM technique has 15% higher DC bus utilization than the SPWM technique. **04**
 - (c) Analyze how the rotor resistance influence the starting and running performance of wound rotor induction motor in context of starting torque and power factor. **07**
- Q.4**
- (a) Define CCM and DCM in context of DC-DC buck converter. **03**
 - (b) How to apply the TRC and CLC methods for output voltage control of chopper fed DC drive? **04**
 - (c) Explain the operation of class C chopper with circuit diagram and waveforms. **07**
- OR
- Q.4**
- (a) State the voltage, current and power polarity in four quadrant chopper with quadrant diagram and application of each quadrant. **03**

- (b) Apply the cyclo-converter to half the speed of 50 Hz single phase induction motor drive. **04**
- (c) Explain the working of three phase VSI with circuit diagram and waveforms of line voltage and phase voltage. **07**

- Q.5** (a) Model the chopper as gain with switching delay and write it's transfer function. **03**
- (b) Analyze the specific torque-speed characteristics of centrifugal fan and pump. **04**
- (c) Explain with block diagram the inner current loop and outer speed loop applied to DC drive. **07**

OR

- Q.5** (a) State the limitations of field weakening method applied to induction motor. **03**
- (b) Analyze the relationship between slip, back EMF, and motor torque during a load-induced speed drop. **04**
- (c) Explain with block diagram how the DC link inverter used for three phase Variable Voltage Variable Frequency control of induction motor. **07**
