

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER- VI EXAMINATION – SUMMER 2026

Subject Code: 3162419

Date:01-06-2026

Subject Name: Principles of Power Supply

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Explain importance of Power Supply in modern electronics applications.	03
	(b) State and explain performance parameters for DC Power. Supply.	04
	(c) Classify filters and explain any one in detail.	07
Q.2	(a) Draw and explain basic block diagram DC power supply.	03
	(b) Explain Op-amp based regulator circuit.	04
	(c) Describe general steps for Power supply design.	07
	OR	
	(c) Explain regulated power supply using LM 723.	07
Q.3	(a) Explain working principle of Switched Mode Power Supply.	03
	(b) Write short note on LM 317.	04
	(c) Explain design of simple regulated power supply based on any suitable IC.	07
	OR	
Q.3	(a) What is the major difference between linear power supply and switch mode power supply?	03
	(b) Explain multiphase buck converter.	04
	(c) Explain any one IC for SMPS control.	07
Q.4	(a) Discuss techniques to improve efficiency in SMPS.	03
	(b) Explain buck converter.	04
	(c) List out various battery charging method and explain anyone.	07
	OR	
Q.4	(a) Explain importance of PCB design for SMPS.	03
	(b) Give the comparison between Lead Acid battery and Li-ion battery.	04
	(c) Explain constant current constant voltage charging in detail.	07
Q.5	(a) Discuss losses and stress in SMPS.	03
	(b) Explain any one control method of SMPS.	04
	(c) Draw and explain block diagram of online and off-line UPS.	07
	OR	
Q.5	(a) Draw and explain block diagram of UPS.	03
	(b) Explain battery-based AC power supply.	04
	(c) Explain power supply for portable electronics equipment.	07
