

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-I (NEW) EXAMINATION – WINTER 2023****Subject Code:3110016****Date:25-01-2024****Subject Name:Basic Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- Q.1** (a) Draw symbol and truth table for AND, NOR, EX-OR logic gates. **03**
- (b) Discuss forward and reverse bias operation of a P-N junction diode with depletion region. **04**
- (c) Draw CB configuration and discuss its input and output characteristics with  $I_{CBO}$ ,  $r_i$ ,  $r_o$ , and current gain  $\alpha$ . **07**
- Q.2** (a) Describe Negative clamper circuit with necessary waveforms **03**
- (b) Describe RC filter with its limitations. **04**
- (c) Draw circuit diagram of Center-taped full wave rectifier and explain its operation with necessary waveforms and derivation of  $V_{dc}$ . **07**
- OR**
- (c) Describe diode approximations in detail. **07**
- Q.3** (a) Draw circuit for Voltage doubler and explain its operation. **03**
- (b) Briefly explain the effect of coupling capacitor and bypass capacitor on small signal transistor amplifier. **04**
- (c) Draw circuit for Emitter feedback bias and explain in detail with its advantages and disadvantages. **07**
- OR**
- Q.3** (a) State the difference between Avalanche breakdown and Zener breakdown. **03**
- (b) Discuss Zener diode as voltage regulator. **04**
- (c) Discuss load line, Q point, DC & AC load lines for BJT. **07**
- Q.4** (a) Derive relation between  $\alpha$  &  $\beta$  for BJT. **03**
- (b) Compare different BJT configurations. **04**
- (c) Describe working principle and applications of PIN Photo diode and Solar cell. **07**
- OR**
- Q.4** (a) Briefly explain regions of operation for BJT. **03**
- (b) Discuss seven segment displays with its types. **04**
- (c) Draw CE configuration and discuss its input and output characteristics with  $I_{CEO}$ ,  $r_i$ ,  $r_o$ , and current gain  $\beta$ . **07**

- Q.5** (a) Compare FET with BJT. **03**  
(b) Explain FET as a switch. **04**  
(c) State different logic families and compare them in terms of fan in, fan out, propagation delay, noise margin, power dissipation. **07**

**OR**

- Q.5** (a) Construct AND & OR gates with diodes. **03**  
(b) Explain FET as an amplifier. **04**  
(c) Explain Drain characteristics and Transfer characteristics of JFET in detail with all related terms as Transconductance  $g_m$ , drain resistance  $r_d$ , and amplification factor  $\mu$ . **07**

\*\*\*\*\*