

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024****Subject Code:3130704****Date:06-07-2024****Subject Name: Digital Fundamentals****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) List out various logic families. Also list characteristics of digital IC.	03
	(b) State and prove De-Morgan's theorems using truth-tables.	04
	(c) Implement AND, OR, EX-OR gates using NAND & NOR gates.	07
Q.2	(a) Reduce the expression $F = x'y'z + yz + xz$	03
	(b) Convert the decimal Number 330.5 to base 4 and base 8.	04
	(c) Design a Combinational circuit that convert Binary to BCD code converter.	07
OR		
	(c) Design a Combinational circuit that convert BCD to Excess 3 code converter.	07
Q.3	(a) Minimize following Boolean function using K-map: $Y(A,B,C,D) = \sum m(0, 1, 3, 5,6, 7, 10, 13,14, 15)$	03
	(b) Explain 4 – bit parallel adder with diagram.	04
	(c) Design 2 - Bit Magnitude Comparator.	07
OR		
Q.3	(a) Design D FF using SR FF. Write truth table of D FF.	03
	(b) Minimize following Boolean function using K-map: $F(A,B,C,D) = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4)$	04
	(c) Design 3-bit even parity generator circuit.	07
Q.4	(a) Compare static RAM and dynamic RAM.	03
	(b) Explain JK flip flop with its characteristic table and excitation table.	04
	(c) Write a brief note on race around condition and its solution. Draw & explain the logic diagram of master-slave JK flip-flop.	07
OR		
Q.4	(a) Explain the types of ROM.	03
	(b) Explain Look-ahead Carry generator	04
	(c) Design a Synchronous counter with the following binary sequence: 0, 1, 3, 4,5, 7 and repeat. Use T – flip-flops	07
Q.5	(a) Explain the working of a Counter.	03
	(b) Explain R-2R ladder type D/A converter	04
	(c) A combinational circuit is defined by the function $F1(A, B, C) = \sum m(0,1,3,4)$ $F2(A, B, C) = \sum m(1,2,3,4,5)$ Implement the circuit with a PLA having 3 inputs, 3 product term & 2 outputs.	07
OR		
Q.5	(a) Explain the working of SISO shift register.	03
	(b) Explain the specification of D/A converter	04
	(c) Describe operation of D/A converter with binary-weighted resistors	07
